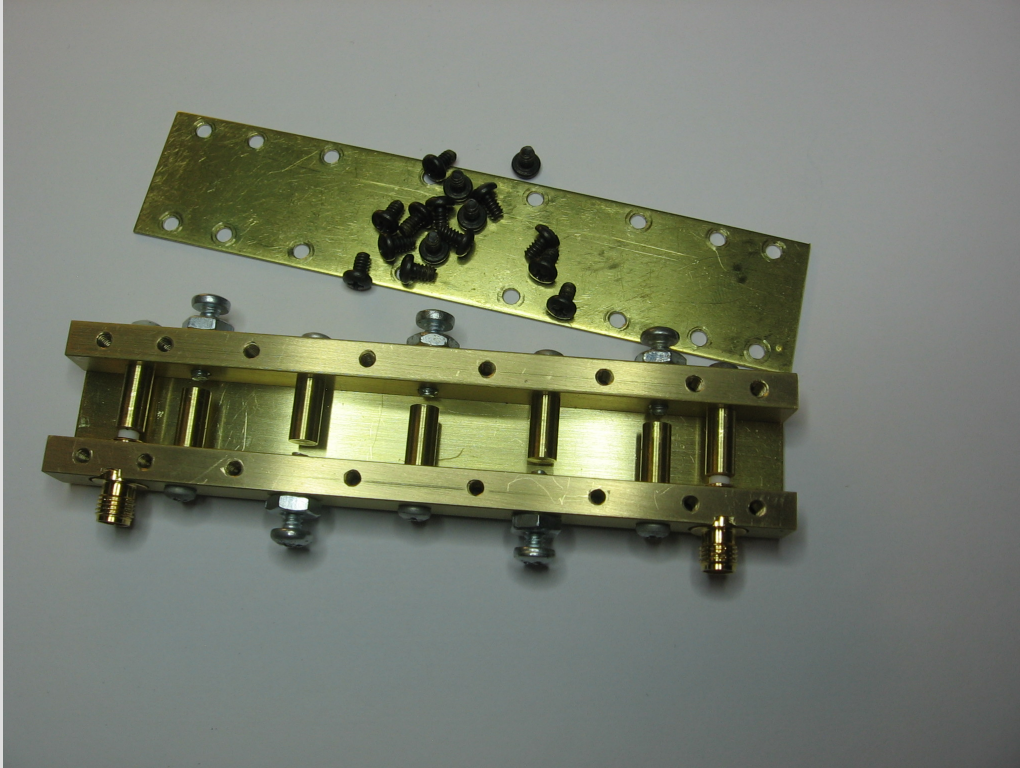


INTRFIL: Design and Construction of Round Rod Interdigitated Filters



Dennis Sweeney WA4LPR
Blacksburg, VA


wa4lpr@arrl.net

Microwave Update 2023
Windsor, CT

INTRFIL: round rod interdigital filter program

- **Exercise to extend the 1985 Ham Radio filter program**
 - HR program made good filters but tap points problematic at high frequency
 - BW and ripple hard to control
 - No upper/lower limit on INTRFIL, usable from 500 to 6000 MHz, maybe beyond
- **Written in Pascal**
 - Source code available under General Public License (GPL)
 - GPL doesn't preclude commercial use but NO warranty, use at own risk
 - Can be freely modified and/or shared but must remain under GPL
 - Anyone want to write a nice GUI for INTRFIL?
 - Intended for anyone to use and not intended or supported as commercial software
 - Executables available or run on Windows, Mac, or Linux with Free Pascal Compiler and Geany IDE (Both available under GPL)

Example Filter

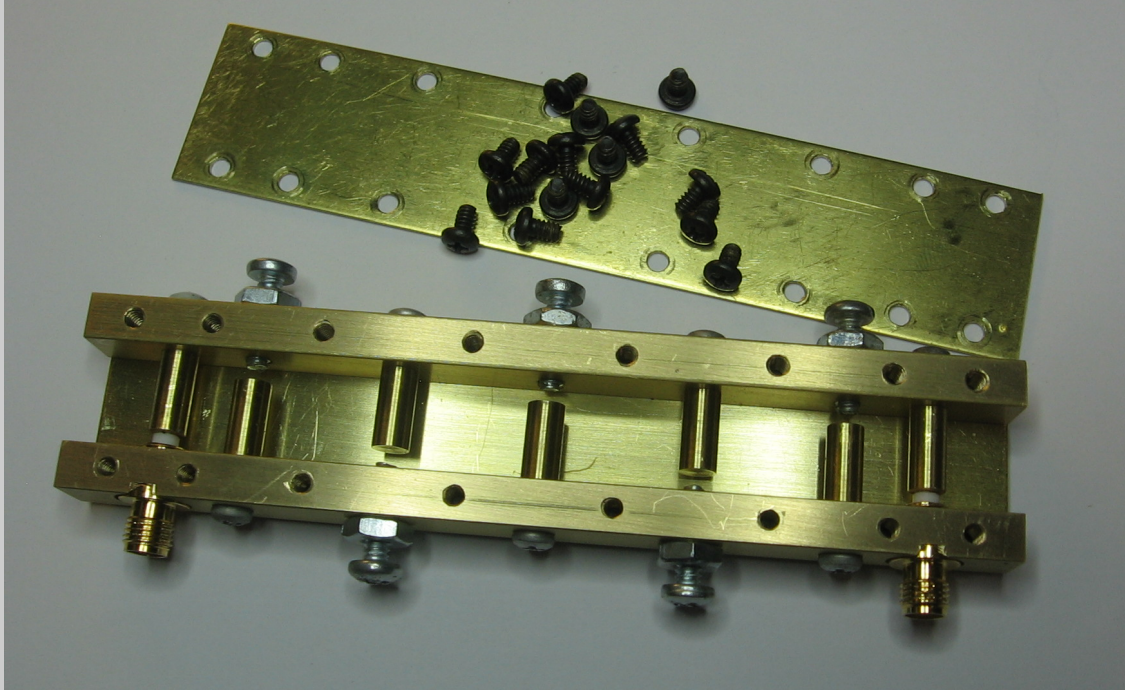

5760 MHz 5 resonator filter
created with INTRFIL

35 MHz (3 dB) bandwidth for
a transverter with 28 MHz IF

Note there are 7 rods. The
end rods are coupling rods

The lid is 1.00 in wide

Overview

- **INTRFIL Example**
 - Running INTRFIL
 - Center Frequency, Adjusting Rod Length and Loss Estimates
 - Error messages
- **QUCS Simulation (Quite Universal Circuit Simulator)**
 - Simulated and Measured results
- **Construction Notes**
- **Inside INTRFIL (time permitting)**

Running INTRFIL

INTRFIL: Interdigitated Filter Program Version 1.0
 Copyright (c) 2021 Dennis G. Sweeney WA4LPR

Number of elements? **5**
 Center frequency (MHz) **5760**
 Butterworth (1) Chebychev (2) ? **2**
 Ripple Bandwidth (MHz) **30**
 Bandpass ripple (DB) **0.05**
 3 dB Bandwidth (MHz) = 35.26 Ripple Return Loss = 19.4 dB
 Load impedance **50**
 ground plane spacing in = **0.375**
 rod dia in = **0.1875**

d/h = 0.500 Slab Zo = 55.76 Co-ax Zo = 56.08

Calculated odd/even impedances and coupling coefficients

Zoo[0] = 46.81	Zoe[0] = 53.19	K = 0.0639
Zoo[1] = 49.62	Zoe[1] = 49.97	K = 0.0035
Zoo[2] = 49.67	Zoe[2] = 49.92	K = 0.0026
Zoo[3] = 49.67	Zoe[3] = 49.92	K = 0.0026
Zoo[4] = 49.62	Zoe[4] = 49.97	K = 0.0035
Zoo[5] = 46.81	Zoe[5] = 53.19	K = 0.0639


**Bold denotes required inputs
 (not in actual program)**

**Calculated 3 dB BW & return
 loss for Chebychev filters**

Slab line impedance

Equivalent coax impedance

Even, Odd Mode Impedances & Coupling

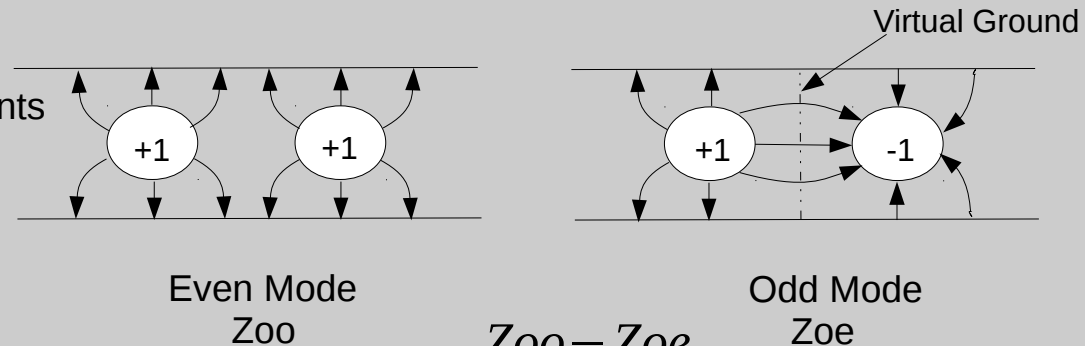

$$K = \frac{Zoo - Zoe}{Zoo + Zoe}$$

Odd/even impedances for fixed $d/h = 0.500$ with s/h rod spacings

$Z_{oo} = 51.92$	$Z_{oe} = 59.01$	$s/h[01] = 0.5953$	$c - c = 0.411$ in
$Z_{oo} = 55.45$	$Z_{oe} = 55.84$	$s/h[12] = 1.4481$	$c - c = 0.731$ in
$Z_{oo} = 55.51$	$Z_{oe} = 55.80$	$s/h[23] = 1.5238$	$c - c = 0.759$ in
$Z_{oo} = 55.51$	$Z_{oe} = 55.80$	$s/h[34] = 1.5238$	$c - c = 0.759$ in
$Z_{oo} = 55.45$	$Z_{oe} = 55.84$	$s/h[45] = 1.4481$	$c - c = 0.731$ in
$Z_{oo} = 51.92$	$Z_{oe} = 59.01$	$s/h[56] = 0.5953$	$c - c = 0.411$ in

Iterative estimate of rod spacing
(Error message possible)

Parameters for filter cavity length = wavelength/4

$C_t = 0.2016$ pf $C_f = 0.1251$ pf $C_p = 0.0765$ pf
 $l = 0.386$ in gap = 0.081 in $\lambda/4 = 0.512$ in

Cap loading & rod length estimate


Cavity spacing width can be adjusted +/- 10% of wavelength/4
Spacing = (in) 0.5

Parameters for Filter cavity

$C_t = 0.1845$ pf $C_f = 0.1251$ pf $C_p = 0.0593$ pf
New C_t Rod Length = 0.395 in New gap = 0.105 in Rod + gap = 0.500 in

Estimated resonator $Q = 1040.2$ Filter $Q = 192.0$
Loss = 5.27 dB

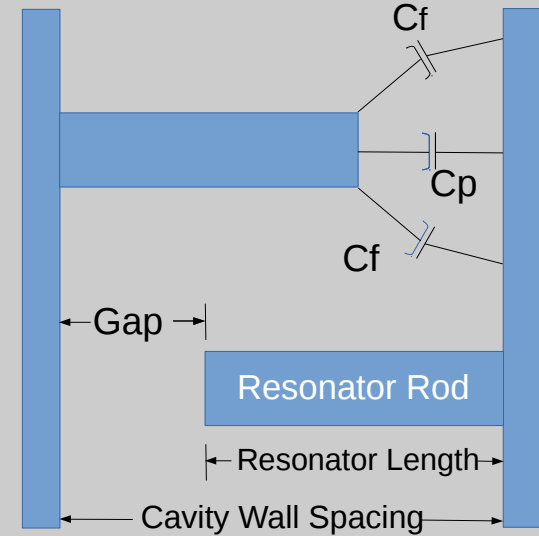Iterative estimate of new cap loading & rod length
(Error message possible)



Loss estimate from filter material

Simulation with QUCS

Data for simulation model using coupled lines

$Z_s = 111.52$

Zooprime = 80.66 Zoepprime = 101.71

Zooprime = 89.40 Zoepprime = 90.54


Zooprime = 89.55 Zoepprime = 90.39

Zooprime = 89.55 Zoepprime = 90.39

Zooprime = 89.40 Zoepprime = 90.54

Zooprime = 80.66 Zoepprime = 101.71

$C_t = 0.1845$ pf Bar length = 10.044 mm

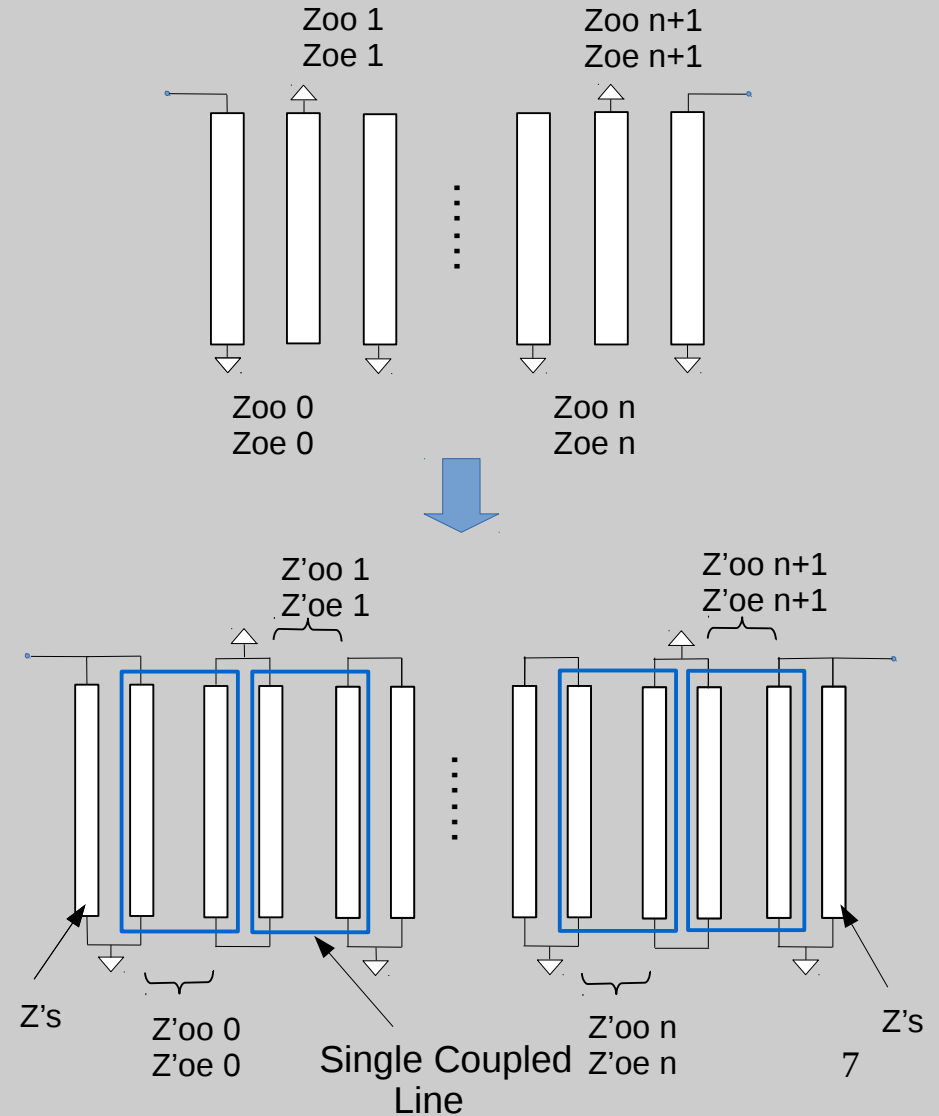


QUCS Simulation

S parameter simulation

SP1
Type=lin
Start=5.66 GHz
Stop=5.86GHz
Points=1001

Equation
Eqn1
 $G = \text{dB}(S[2,1])$


Equation
Eqn2
 $RL = \text{dB}(S[1,1])$

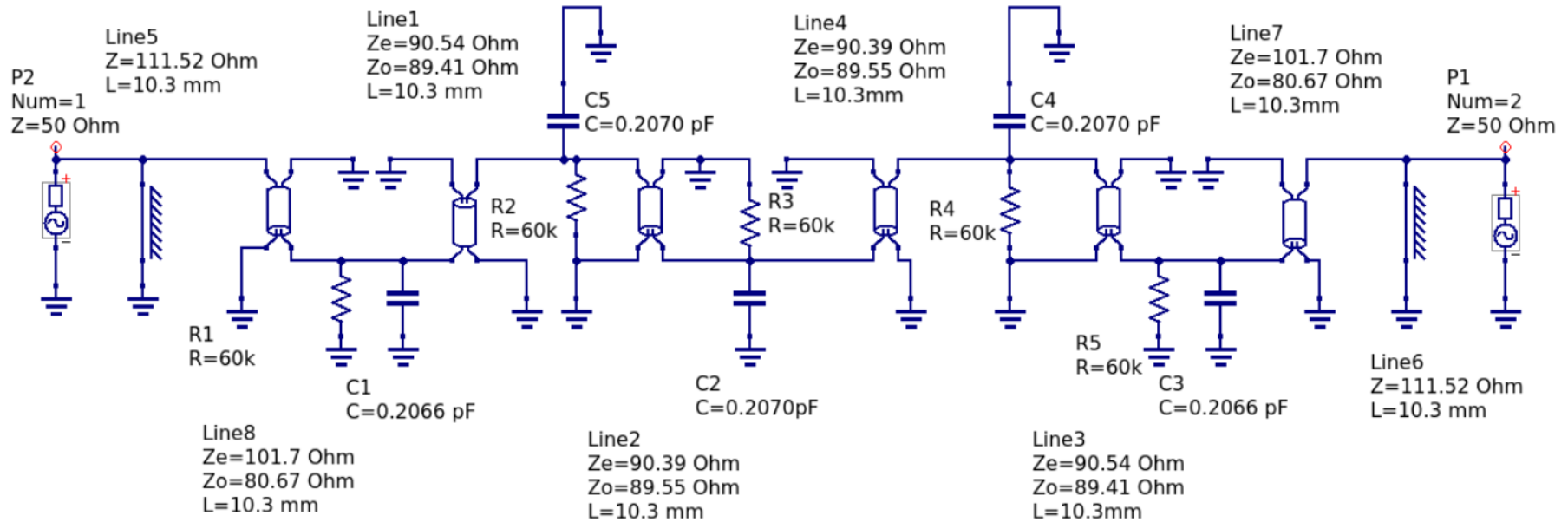


Center frequency trimmed with C1-C5

Lines lengthened 2.5%



Loss added with R1-R5

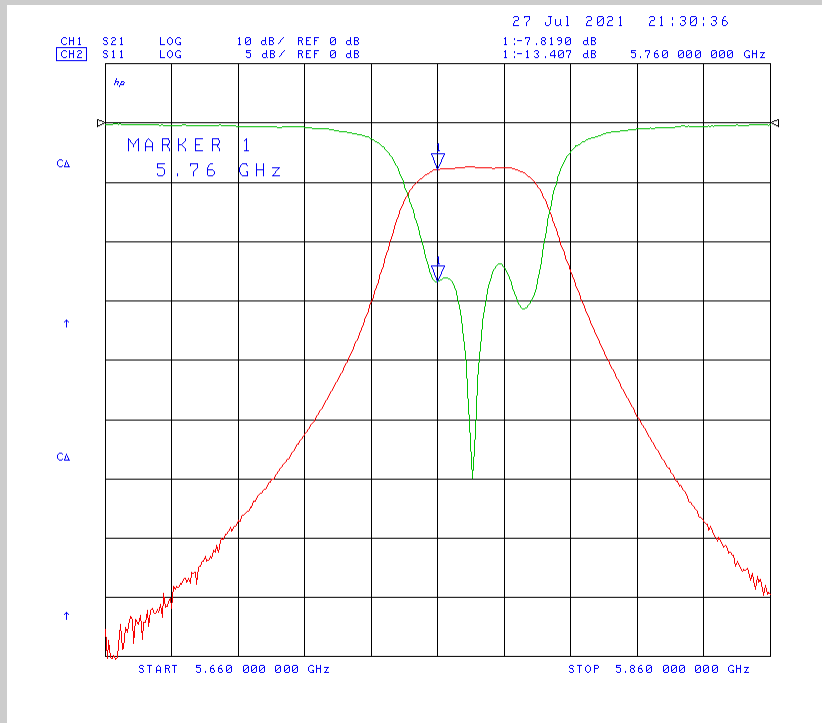

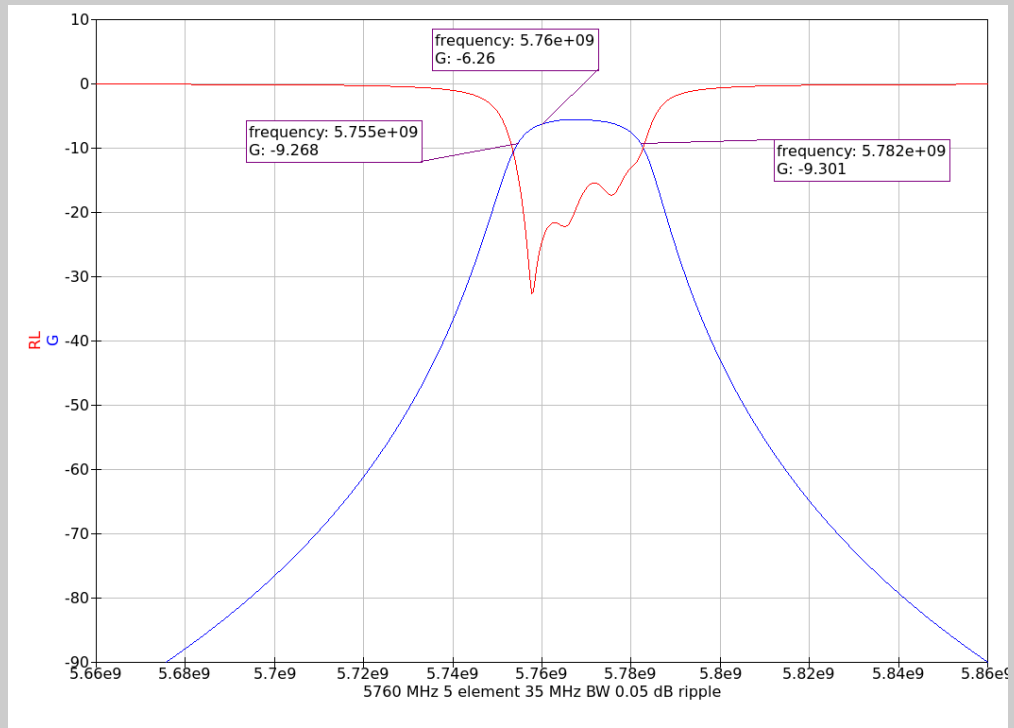Measured Insertion & Return Loss.
 3 dB BW = 36.96 MHz (calculated 35.26 MHz)
 Midband Loss = 7.5 dB (calculated 6.27 dB)
 33.4 dB dwn @ 28 MHz removed
 56.5 dB dwn @ 56 MHz removed



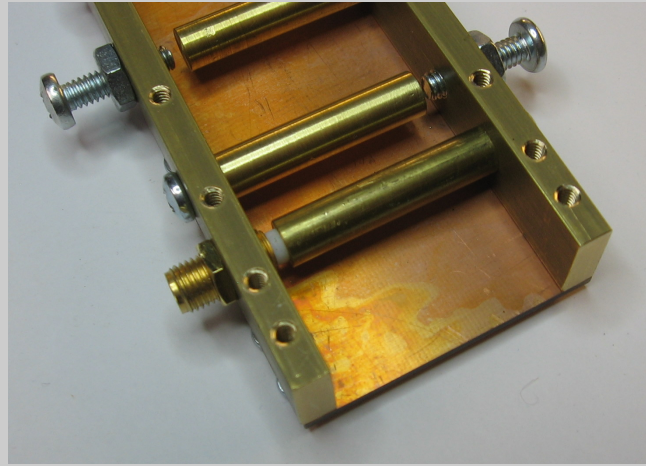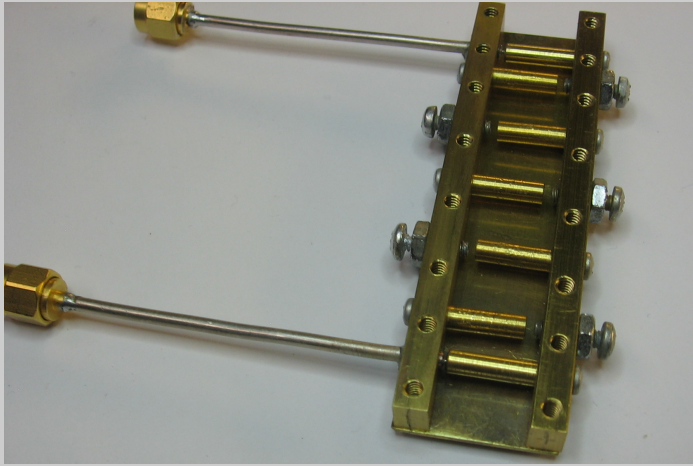Simulated Insertion & Return Loss.
 3 dB BW = 27 MHz
 Midband Loss = 6.26 dB.
 INTRFIL Center frequency tends to be high,
 rods lengthened 2.5% & tuned to 5760 MHz





Construction Notes

- **Test filters made with a table top milling machine & lathe**
 - Screws $\frac{1}{2}$ way between each bar and ends open after a couple of diameters
- **SMA connectors screwed in (1/4-36 tap) or 0.85" coax soldered in sidewalls**
- **d/h = 0.5 convenient with standard sized material**
 - bars & rods obtained from www.onlinemetals.com
- **Walls made with K&S brass strips, PCB material & 0.05" AL sheet**
- **Simpler methods with K&S strips and 0.141 coax rods?**

Inside INTRFIL

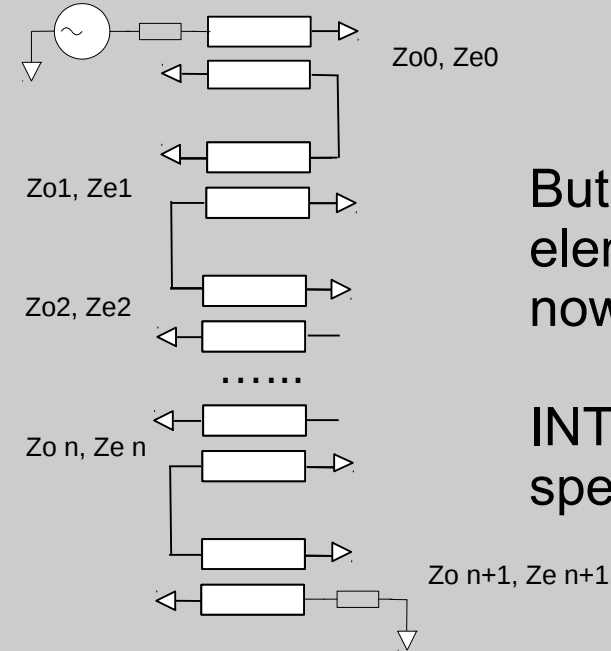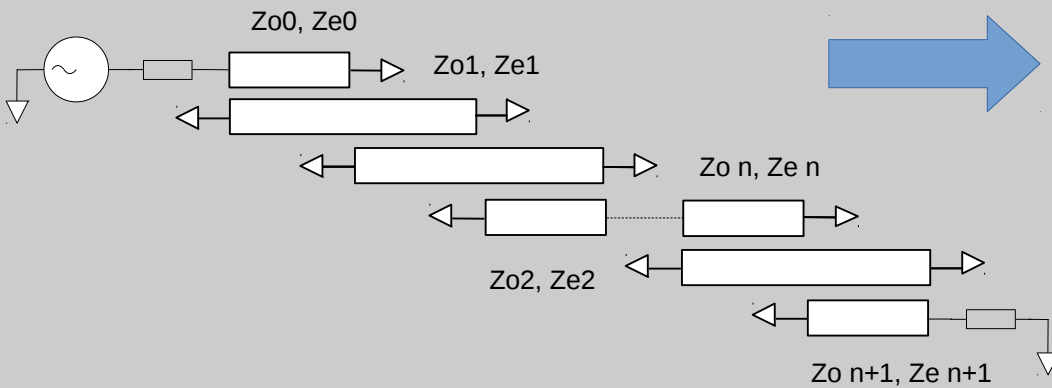
Matthaei edge coupled filter (reference in paper) folded in half for an interdigitated structure



But doubles BW,
elements in series
now in parallel

INTRFIL divides
specified BW by 2

Inside INTRFIL

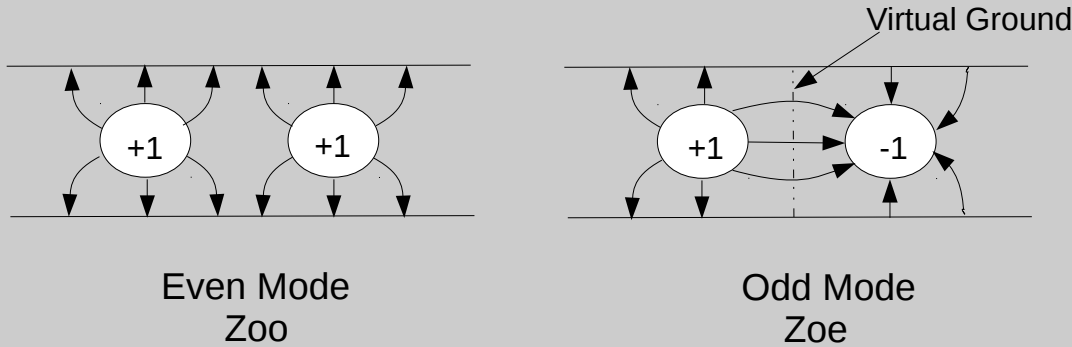

$$K = \frac{Z_{oo} - Z_{oe}}{Z_{oo} + Z_{oe}}$$

d/h is fixed and s/h adjusted to produce calculated value of K .

K is a function of Z_{oo}/Z_{oe} which are complex functions of d/h and s/h :

$$K = f(Z_{oo}/Z_{oe}) = f(d/h, s/h)$$

An iterative algorithm determines s/h for a given K with d/h fixed but may not converge for some values of K , BW or ripple. INTRFIL reports a “failed to converge” error. Small changes in BW or ripple usually fixes this.

In Summary

- **INTRFIL more complex than hairpin or pipe cap filters but much higher performance particularly in the stopband.**
 - Stopband performance important in reducing out of band emissions and mutual interference when groups of microwavers gather
 - 3 and 5 element filters for 1.3, 2.3 & 5.7 GHz made with INTRFIL
- **Detailed paper with 2.3 & 5.7 GHz filters to be published in QEX**
 - Referenced papers available
 - Mechanical drawings

Getting INTRFIL

- **Source and executables available from me or Blue Ridge Microwave Society group site: groups.io/g/brms**
 - Must register to see “Files” folder
 - Version 1.1 edited to output metric dimensions
 - All internal calculation done in cm
 - MUD 1989 WGFIL waveguide filter program is also available on BRMS (executable and Pascal source)