

SR Lite RX V6.2 40/30m 04_Operational Amplifiers


[Home](#) [Bill of Materials](#) [Power Supply](#) [Local Oscillator](#) [Dividers](#) [Operational Amplifiers](#) [BPF](#) [Mixer](#) [External Connections](#) [Comments](#) [Revisions as of 12/14/2008](#) [WB5RVZ Main Homepage](#)

Operational Amplifiers Introduction

Operational Amplifiers Schematic

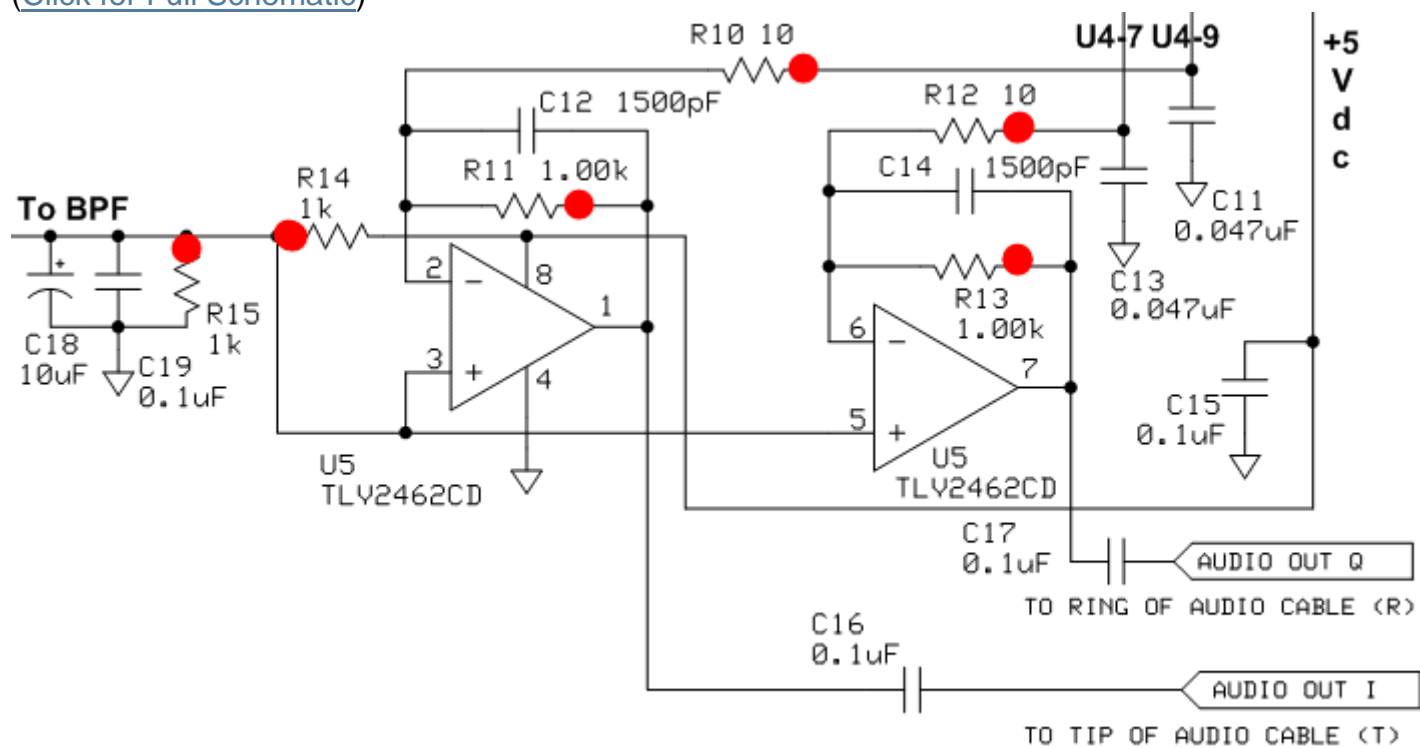(Resistor testpoints (hairpin, top, or left-hand lead), as physically installed on the board, are marked in the schematic with red dots)




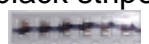






[\(Click for Full Schematic\)](#)




Operational Amplifiers Bill of Materials

Detailed Bill of Materials

Check	Designation	Component	Marking	Category	Orientation	Notes	Circuit
-------	-------------	-----------	---------	----------	-------------	-------	---------
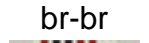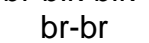
<input type="checkbox"/>	C11	0.047 uF 5%	473	Ceramic			Operational Amplifiers
<input type="checkbox"/>	C12	1500 pF 10%	152	Ceramic			Operational Amplifiers
<input type="checkbox"/>	C13	0.047 uF 5%	473	Ceramic			Operational Amplifiers
<input type="checkbox"/>	C14	1500 pF 10%	152	Ceramic			Operational Amplifiers
<input type="checkbox"/>	C15	0.1 uF	black stripe 	SMT 1206			Operational Amplifiers
<input type="checkbox"/>	C16	0.1 uF	black stripe 	SMT 1206			Operational Amplifiers
<input type="checkbox"/>	C17	0.1 uF	black stripe 	SMT 1206			Operational Amplifiers
<input type="checkbox"/>	C18	10uF/16 VDC		Electrolytic			Operational Amplifiers
<input type="checkbox"/>	C19	0.1 uF	black stripe 	SMT 1206			Operational Amplifiers
<input type="checkbox"/>	Cxx	4.7 uF 10%	475	Ceramic		for audio test	Operational Amplifiers
<input type="checkbox"/>	R10	10 ohm 1/4W 1%	br-blk-blk- gl-br 	1/4W	W-E		Operational Amplifiers
<input type="checkbox"/>	R11	1 k 1/4W 1%	br-blk-blk- br-br 	1/4W	E-W		Operational Amplifiers
<input type="checkbox"/>	R12	10 ohm 1/4W 1%	br-blk-blk- gl-br 	1/4W	S-N		Operational Amplifiers
<input type="checkbox"/>	R13	1 k 1/4W 1%	br-blk-blk- br-br 	1/4W	E-W		Operational Amplifiers
<input type="checkbox"/>	R14	1 k 1/4W 1%	br-blk-blk- br-br 	1/4W	W-E		Operational Amplifiers
<input type="checkbox"/>	R15	1 k 1/4W 1%	br-blk-blk- br-br 	1/4W	W-E		Operational Amplifiers
<input type="checkbox"/>	U5	TVL2462CD dual opamp	TVL2462CD	SOIC-8			Operational Amplifiers

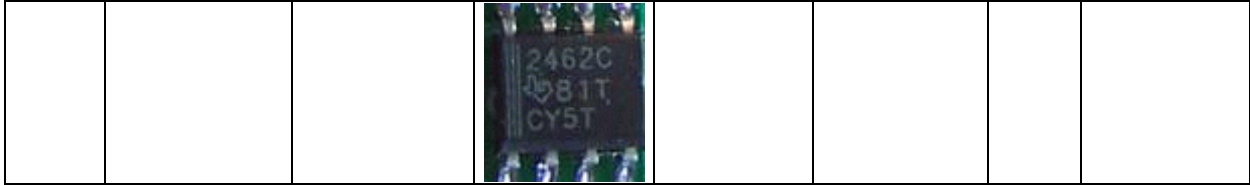


Operational Amplifiers Summary Build Notes

- Install U5, Dual OpAmp
- Install SMT Caps
- Install Topside SMT Cap
- Install Ceramic Caps
- Install Electrolytic Cap
- Install Resistors
- [Test the Stage](#)


Operational Amplifiers Detailed Build Notes

Bottom of the Board

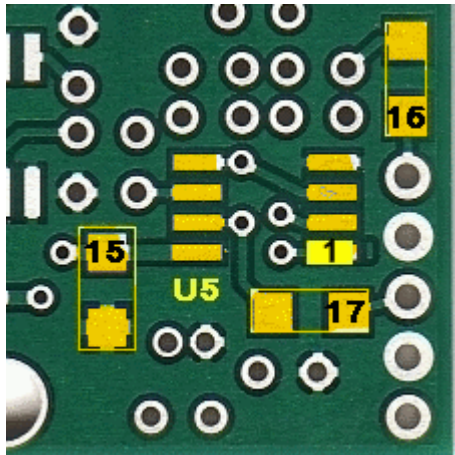




Install U5, Dual OpAmp


Orient U5 on its pads so that the pin 1 corner of the IC matches the small "1" (it also looks like a "0") mark in the copper on the bottom side of the board. In general, pin 1 of an SOIC packaged IC is in the lower left corner of the package when the printing on the package top reads upright, from left to right. Tack-solder one corner pin of U5 and reheat the tacked pin as necessary to line up U5 on its pads properly. Double-check the orientation of U5 and the line up of the IC on its pads with magnification and good lighting. You do NOT want to install U5 oriented incorrectly. If all is well, carefully solder the rest of the leads to their pads.

Check	Designation	Component	Marking	Category	Orientation	Notes
<input type="checkbox"/>	U5	TVL2462CD dual opamp	TVL2462CD 	SOIC-8		Take ESD precautions


Install SMT Caps

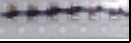Check	Designation	Component	Marking	Category	Orientation	Notes
<input type="checkbox"/>	C15	0.1 uF	black stripe 	SMT 1206		
<input type="checkbox"/>	C16	0.1 uF	black stripe 	SMT 1206		
<input type="checkbox"/>	C17	0.1 uF	black stripe 	SMT 1206		

Top of the Board

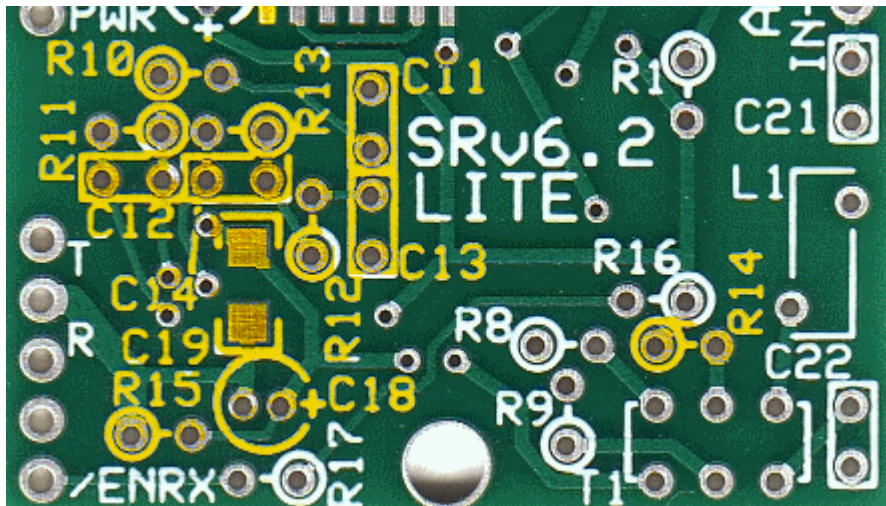

Install Topside SMT Cap

Check	Designation	Component	Marking	Category	Orientation	Notes
<input type="checkbox"/>	C19	0.1 uF	black stripe 	SMT 1206		

Install Ceramic Caps

Check	Designation	Component	Marking	Category	Orientation	Notes
<input type="checkbox"/>	Cxx	4.7 uF 10%	475	Ceramic		for audio test
<input type="checkbox"/>	C11	0.047 uF 5%	473	Ceramic		
<input type="checkbox"/>	C12	1500 pF 10%	152	Ceramic		
<input type="checkbox"/>	C13	0.047 uF 5%	473	Ceramic		
<input type="checkbox"/>	C14	1500 pF 10%	152	Ceramic		






Install Electrolytic Cap

C18 is installed with attention paid to ensuring the positive lead (the longest lead) goes to the positive (“+”) hole.

Check	Designation	Component	Marking	Category	Orientation	Notes
<input type="checkbox"/>	C18	10uF/16 VDC		Electrolytic		

Install Resistors


Finally, install the five resistors (R10-R14) on the top side of the board. Note that R14 and R16 could be confused: R14 lies below R16:

 Check	Designation	Component	Marking	Category	Orientation	Notes
<input type="checkbox"/>	R10	10 ohm 1/4W 1%	br-blk- blk-gl-br 	1/4W	W-E	
<input type="checkbox"/>	R11	1 k 1/4W 1%	br-blk- blk-br-br 	1/4W	E-W	
<input type="checkbox"/>	R12	10 ohm 1/4W 1%	br-blk- blk-gl-br 	1/4W	S-N	
<input type="checkbox"/>	R13	1 k 1/4W 1%	br-blk- blk-br-br 	1/4W	E-W	
<input type="checkbox"/>	R14	1 k 1/4W 1%	br-blk- blk-br-br 	1/4W	W-E	


						
<input type="checkbox"/>	R15	1 k 1/4W 1%	br-blk- blk-br-br	1/4W	W-E	

Operational Amplifiers Completed Stage

Top of the Board

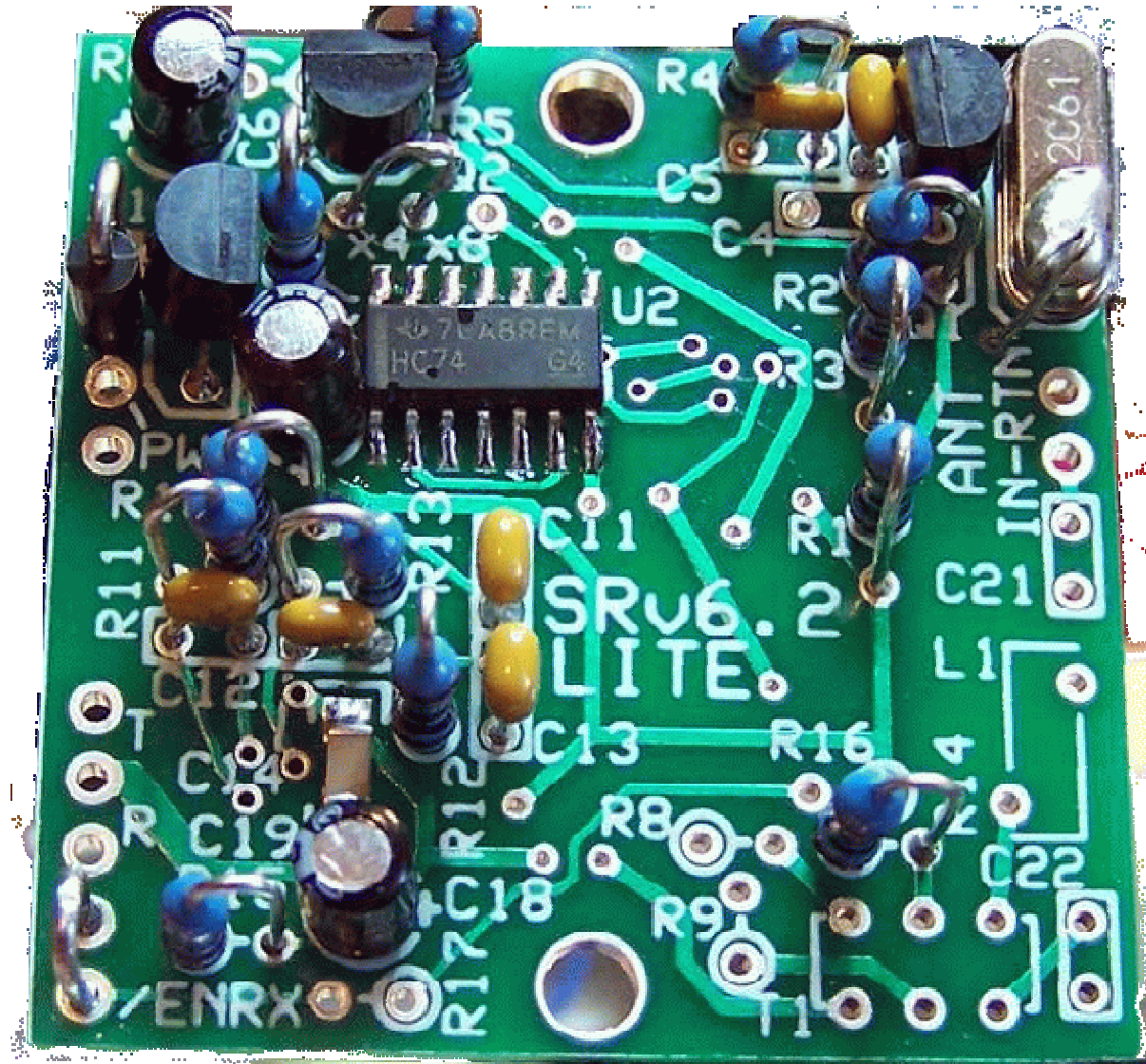

Bottom of the Board

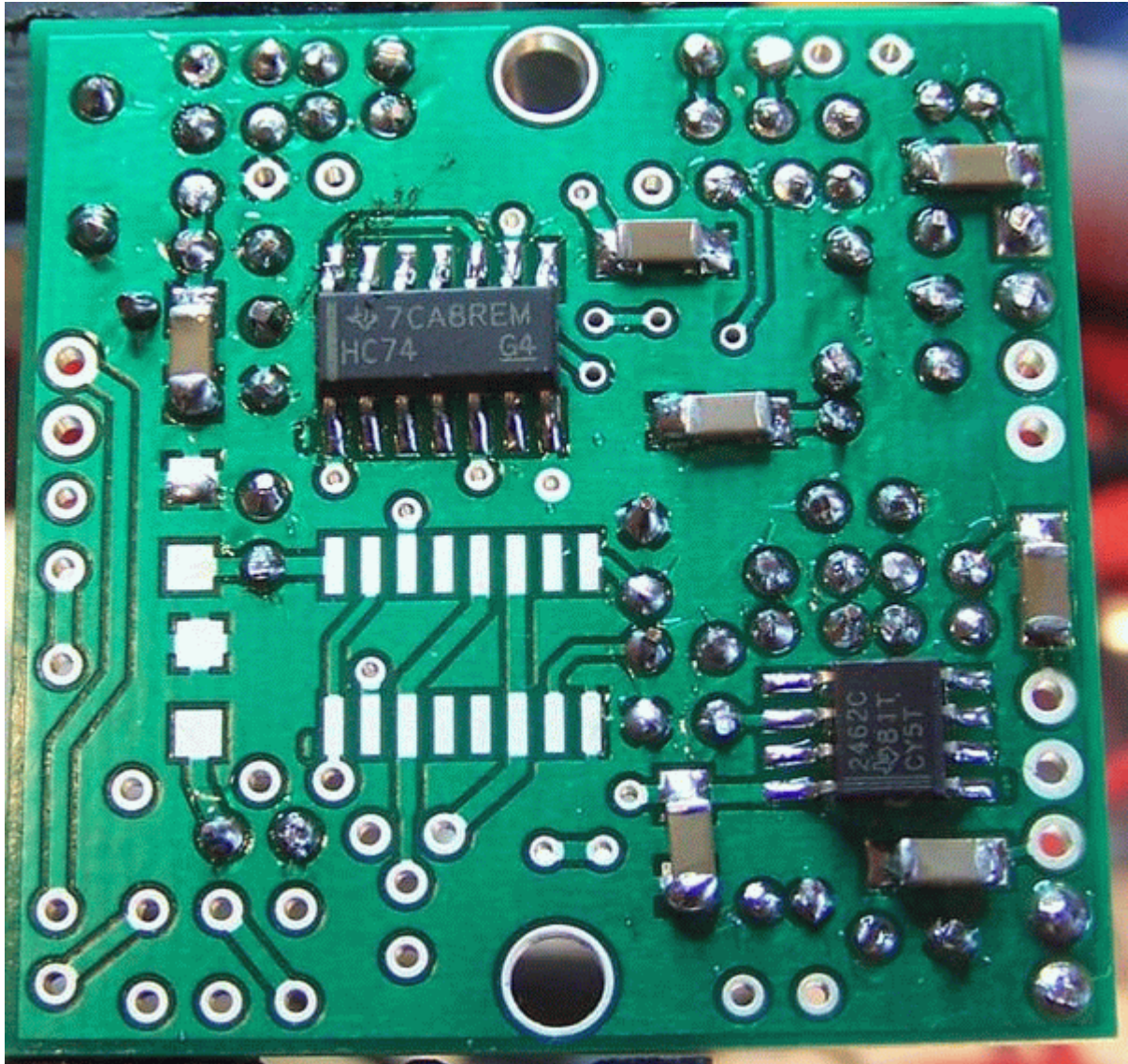

Operational Amplifiers Testing

Warning

Test Setup

Take appropriate ESD precautions in these tests, since you will be working around the sensitive OpAmp IC

Visual Inspection

Test Setup

Using very good lighting and magnification, carefully inspect the solder joints to identify bridges, cold joints, or poor contacts.

Pay especial attention to the joints on the OpAmp IC pins. If necessary, touch up the joints with your iron and/or some flux. Wick up any excess.

Current Draw

Test Setup

- connect a 1k ohm resistor in series with the positive power lead
- apply 9 Vdc and measure the current draw with the limiting resistor in place
- remove the current limiting resistor
- apply 9 Vdc and measure the current draw without the limiting resistor

Test Measurements

Testpoint	Units	Nominal Value	Author's	Yours
Current draw WITH 1k ohm current limiting resistor	mA	< 9	6.1	
Current draw without the limiting resistor	mA	25-35	28.1	


IC Pin Voltages

Test Setup

In addition to using the convenient test points indicated in the table below, you should also double check by measuring the voltages on the actual IC pins (to detect the case of a poor or missing solder joint between the pin and the pad.

expected voltages are indicated in the table below:

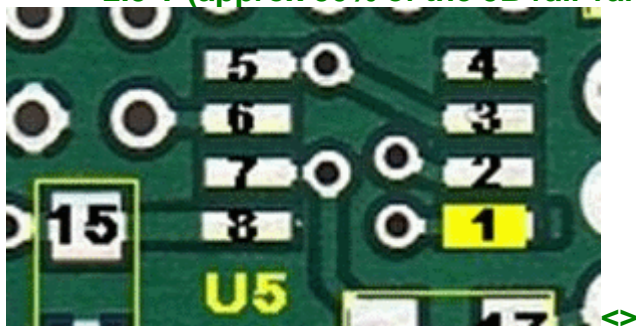- 5 V (range of 4.5 - 5.4)
- 2.5 V (approx 50% of the 5B rail value)



Test Measurements

Testpoint	Units	Nominal Value	Author's	Yours
pin 1	Vdc	2.5	2.48	_____
pin 2	Vdc	2.5	2.48	_____
pin 3	Vdc	2.5	2.48	_____
pin 4	Vdc	0	0	_____
pin 5	Vdc	2.5	2.48	_____
pin 6	Vdc	2.5	2.48	_____
pin 7	Vdc	2.5	2.48	_____
pin 8	Vdc	5	4.94	_____

Op Amp Function Test

Test Setup

You can test the functioning of both of the op-amps by comparing the pin-out voltages under different input resistance measurements. The test requires you to have a 1.5 k Ohm to 3.3 k Ohm resistor (of any wattage or precision) that you can temporarily connect to the circuit. The author used an available 2.2 k Ohm resistor.

- Power up the circuit and measure the voltage at pin 1 of the op-amp (hairpin of R11). It should be ~2.5 Vdc
- Power off and use clip leads to connect a 2.2 k Ohm resistor (R_t) between the hairpin of R10 and circuit ground. (This provides an input resistance R_i) of 2210 ohms to the op-amp. Power up and measure the voltage at the hairpin of R11. You should get ~3.74 Vdc.
- Remove R_t and the output voltage should go back to ~2.5 Vdc.
- Perform the same test for op-amp 2, substituting R12 for R10 and R13 for R11

An [Excel spreadsheet](#) with a calculator for this test is available for you to plug in your bridging resistor ohms (R_t) and your pin 1 or pin 7 normal voltages (E_{bias}) and predict the expected voltage when bridged (E_{out}).

Test Measurements

Testpoint	Units	Nominal Value	Author's	Yours
Normal pin 1 (R1 not connected)	Vdc	2.4 - 2.5	2.5	_____
pin 1 bridged with 2.2k resistor	Vdc	3.6 - 3.75	3.63	_____
normal pin 7	Vdc	2.4 - 2.5	2.5	_____
pin 7 bridged with 2.2k resistor	Vdc	3.6 - 3.75	3.63	_____

[Home](#) [Bill of Materials](#) [Power Supply](#) [Local Oscillator](#) [Dividers](#) [Operational](#)
[Amplifiers](#) [BPF](#) [Mixer](#) [External Connections](#) [Comments](#) [Revisions as of](#)
[12/14/2008](#) [WB5RVZ Main Homepage](#)